

**Academy of Innovative Semiconductor and Sustainable Manufacturing**

**ANALOG INTEGRATED CIRCUIT DESIGN AND LAYOUT LAB**

**MOSFET CHARACTERISTIC CURVE**

Student: Pham Lo Hoang Khang

Student ID: XZ4138222

Group: B1

## LAB2-1-4. INVERTER TRANSIENT WAVEFORM

Parameter:

.subckt INV in out vdd gnd

MM1 in out vdd vdd P\_18 W=6.8u L=0.18u m=2

MM2 in out gnd gnd N\_18 W=2u L=0.18u m=2

.ends

LAB2_1_4.sp		INV.cir
subckt	xinv1	xinv1
element	1:m1	1:m2
model	0:p_18.1	0:n_18.1
region	Linear	Cutoff
id	-44.541217p	37.341165p
ibs	6.47085e-27	-1.26652e-26
ibd	7.40756e-24	-1.070830f
vgs	-1.800000	0.
vds	-7.804781n	1.800000
vbs	0.	0.
vth	-528.450300m	463.164469m
vdsat	-927.415768m	53.208422m
vod	-1.271550	-463.164469m
beta	6.712453m	7.931224m
gam_eff	557.084657m	507.445914m
gm	18.715164p	1.225275n
gds	5.716894m	28.095903p
gmb	9.952535p	182.035537p
cdtot	40.974837f	4.787874f
cgtot	30.478874f	4.560853f
cstot	39.615562f	6.519503f
cbtot	33.954846f	9.655385f
cgs	15.448926f	1.553244f
cgd	14.881572f	1.553200f

\*\*\*\*\*  
\* testbench for mos characteristic \*  
\*\*\*\*\* transient analysis tnom= 25.000 temp= 27.000 \*\*\*\*\*  
vmax= 1.839554 at= 10.033833n  
from= 0. to= 100.000000n  
vmin= -19.702757m at= 40.131790n  
from= 0. to= 100.000000n  
trise= 94.722757p targ= 40.263272n trig= 40.168550n  
tfall= 94.210498p targ= 30.169511n trig= 30.075301n  
trise\_tfall\_diff %= 542.264698m  
tplh= 55.191856p targ= 20.205192n trig= 20.150000n  
tphl= 68.767887p targ= 30.118768n trig= 30.050000n

Filter: ▾  ▾









 
-  temper=27
-  tfall=94.2p
-  tphl=68.8p
-  tplh=55.2p
-  trise=94.7p
-  trise\_tfall\_diff\_%=542m
-  vmax=1.84
-  vmin=-19.7m

Figure 1. Spec



### Comment:

- *Fall Time (tfall): 94.2 ps*

\* Increase tfall by:

- Decreasing the W/L ratio of the NMOS transistor. This reduces its drive strength, slowing down the discharge rate of the output capacitance.

- *Rise Time (trise): 94.7 ps*

\* Increase trise by:

- Decreasing the W/L ratio of the PMOS transistor. This reduces its drive strength, slowing down the charge rate of the output capacitance.

- *High-to-Low Propagation Delay (tphl): 68.8 ps*

\* Time for the output to switch from high to low after the input changes. Influenced by the NMOS transistor's drive strength and load conditions.



- *Low-to-High Propagation Delay (tplh): 55.2 ps*

\* Time for the output to switch from low to high after the input changes. Influenced by the PMOS transistor's drive strength and load conditions.


- *Rise to Fall Time Difference (trise\_tfall\_diff%): 0.542%*

\* Decrease trise\_tfall\_diff% by:

  - Balancing the W/L ratios of the PMOS and NMOS transistors to ensure symmetrical drive strengths. Fine-tuning the W/L ratios so that the drive strengths of both transistors match, resulting in similar rise and fall times.



\*/

 

*Figure 2. Output Waveform*

**Comment:**

- When  $V_i = 0$ , the NMOS is off, the PMOS is on,  $V_{out}$  is up to 1.8V.
- When  $0 < V_i < V_{TH}$ : the NMOS is off, the PMOS is on,  $V_{out}$  is pulled up close to  $V_{dd}$ , but may drop slightly due to voltage drop across the PMOS.
- When  $V_i$  is approximately  $V_{TH}$ , the NMOS is on, the PMOS is off,  $V_{out}$  starts converting from  $V_{dd}$  to GND.
- When  $V_{TH} < V_i < (V_{dd} - V_{TH})$ , the NMOS is on, the PMOS is off,  $V_{out}$  is pulled down close to GND, but there may be a slight positive voltage due to the voltage drop across the NMOS.
- When  $V_i$  is approximately  $V_{dd}$ , the NMOS is on, the PMOS is off,  $V_{out}$  is 0 (GND).
- With H Cursor, the intersection position between  $V_{in}$  and  $V_{out}$  is at  $V_{in} = 910\text{mV}$ . We want that intersection point to be located exactly at the position  $V_{dd}/2 = 900\text{mV}$ .

--- END ---