

Academy of Innovative Semiconductor and Sustainable Manufacturing

ANALOG INTEGRATED CIRCUIT DESIGN AND LAYOUT LAB

TWO STAGE OPAMP

Student: Pham Lo Hoang Khang

Student ID: XZ4138222

Group: B1

LAB2-3: SINGLE-ENDED DIFFERENTIAL TWO-STAGE OPAMP

```

*****
.subckt opamp vip vin vout vdd gnd vb1 vbr
*****
$ write your stage1+stage2 here

*Stage1
m05 n0 vb1 vdd vdd p_18 l=0.18u w=2.48u m=4
m01 vbn vin n0 n0 p_18 l=0.68u w=6.06u m=4
m02 von1 vip n0 n0 p_18 l=0.68u w=6.06u m=4
m03 vbn vbn gnd gnd n_18 l=3.50u w=4.37u m=2
m04 von1 vbn gnd gnd n_18 l=3.50u w=4.37u m=2
*Stage2
m06 vout vb1 vdd vdd p_18 l=0.20u w=5.60u m=8
m07 vout von1 gnd gnd n_18 l=0.31u w=4.60u m=4
*****
$ Bias (external)
* vvb1 vb1 gnd 1.17
* vvbr vbr gnd 1.17
*****
$ write your zero compensation here
ccp vout nrcp 0.3p
m16 nrcp vbr von1 gnd n_18 l=0.21u w=1u m=4
*****
.ends

```

Figure 1. Opamp Parameter

	AC_sim_template.sp	DC_sim_template.sp	TRAN_sim_template.sp	AC_sim_template.li
cbtot	69.7462736689f	97.6755980133f	47.9407074687f	9.6037598848f
cgs	184.5437826888f	62.2112066731f	35.6003173518f	2.1947077921f
cgd	3.0572596493f	15.9980922456f	6.6760043334f	2.2434400131f


```

*****
* single-ended differential two-stage opamp design ****

***** ac analysis tnom= 25.000 temp= 27.000 *****
gain= 67.4658020652 at= 1.0000000000
      from= 1.0000000000 to= 100.0000000000g
gbw= 173.9581078666x
phase=-113.6705215700
phase_margin= 66.3294784300
power_avg= 470.1166950120u from= 1.0000000000 to= 100.0000000000g

```

Figure 2. Gain, Bandwidth, Phase, Phase Margin & Power Consumption

```

**info** set option symb=1 internally to help for convergence.
*****
***** option summary
*****
runlvl = 5          bypass = 2.0000000000
Opening plot unit= 15
file=DC_sim_template.pa0

*****
* single-ended differential two-stage opamp design ****

***** dc transfer curves tnom= 25.000 temp= 27.000 *****
top_gain= 3.3630955630k
bottom gain= 3.0643893203k
power_avg= 308.2543604534u from= 850.0000000000m to= 950.0000000000m
**info** dc convergence successful at Newton-Raphson method
*****
* single-ended differential two-stage opamp design ****

***** operating point information tnom= 25.000 temp= 27.000 *****
***** operating point status is all simulation time is 0.
node =voltage node =voltage

+0:vb1 = 1.1700000000 0:vbr = 1.1700000000
+0:vdd = 1.8000000000 0:vin = 1.8000000000
+0:vip = 0. 0:vo = 11.8842182429m
+1:n0 = 1.7999998184 1:nrcp = 1.0840905013
+1:vbn = 18.0759881697m 1:von1 = 1.7999997870

```

Figure 3. Top gain and Bottom gain

```

*****
* single-ended differential two-stage opamp design ****

***** transient analysis tnom= 25.000 temp= 27.000 *****
sr_rate= 84.2183109219x
power_avg= 457.3257141551u from= 0. to= 10.0000000000u

```

Figure 4. Slew rate

 


Figure 5. Bode plot of Opamp

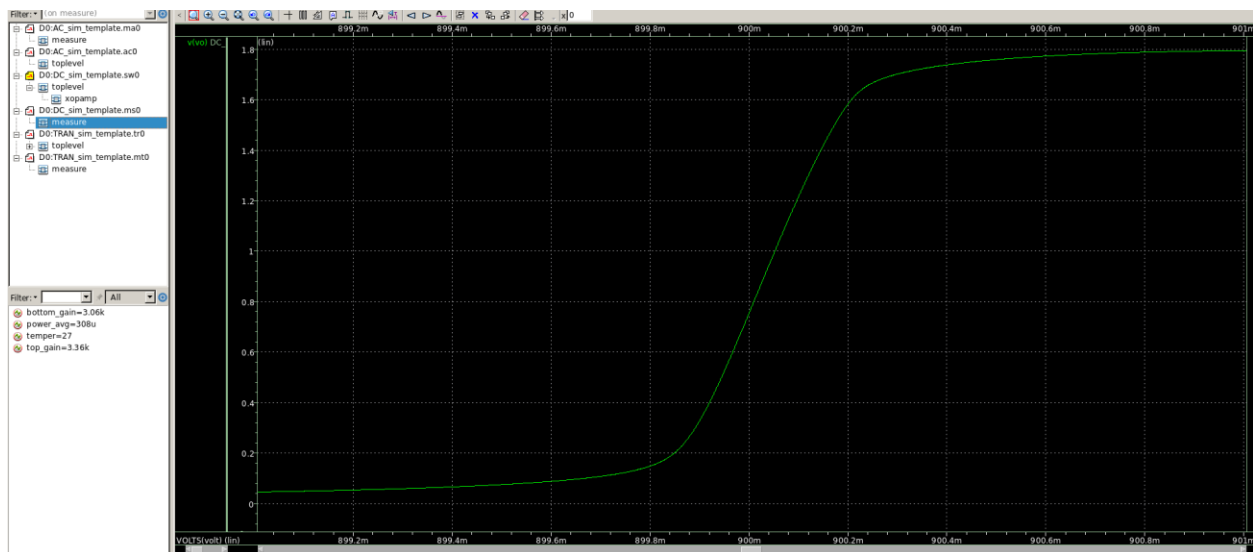


Figure 6. Output Swing of Opamp

 


Figure 7. Slew rate of Opamp

Comment:

First, I noticed that the slew rate is low, so to increase the slew rate, I need to increase the drain current (I_D), which means increasing the width (W). However, increasing W has its limits in stage 2, as excessively increasing W does not significantly enhance the slew rate. Therefore, I reduce the value of the compensation capacitor (C_C) to increase the slew rate and simultaneously increase the bandwidth, but this also reduces the Phase margin. When trading off these values, I finally achieve results that meet the specifications.

--- END ---